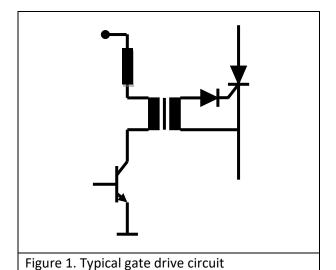


Thyristor Gate Drives

AN6148-1 June 2014 (LN31657)

Introduction

The output of the electronics that control the sequence of firing of thyristors is at logic level of a few volts, negligible current and usually at ground potential. The thyristors require a firing signal that is tens of volts and tens to hundreds of milliamps. In addition the thyristor is often at a high potential above ground. The circuit that links these disparate conditions is the gate drive circuit. The purpose of the gate drive circuit is to provide a current pulse of the required shape, peak value, duration and frequency when prompted by the output from the control electronics. Also the outputs from the gate drives invariably have to be isolated from one another because the thyristors in a converter normally have potentials that differ by many hundreds of volts. This isolation is realised with the use of pulse transformers as shown in figure 1.




Usually triggering is inhibited when the anode voltage of the thyristor is negative. This is because, in this mode, the thyristor acts like a low gain transistor and amplifies the gate current which is seen as an increase in anode leakage current. This together with the blocking voltage across the device gives a significant increase in power dissipation in the thyristor. This extra power loss has to be considered when dimensioning the heatsinks otherwise the device can overheat. But perhaps its most significant effect is associated with series connected thyristors where the increase in leakage current can make achieving voltage sharing between the thyristors much more difficult.

Trigger current shape

Whilst almost any shape of current pulse will turn a thyristor into conduction as long as it exceeds the Vgt and lgt values given in the datasheet, thyristors experience high rates of rise of anode/cathode current from the discharge of the R-C snubber circuit every time the thyristor is fired and from the commutation of other thyristors in the converter. Additionally, if thyristors are connected in series or parallel. thyristors in an arm of the converter need to be turned on together. This reduction in delay time and the ability to receive a high di/dt is enhanced by the gate current pulse having a sharply rising front edge with a rate of rise in excess of 1A/µs, and a peak value of 5 to 10 times the lgt value. The rate of rise of the current is determined by the stray inductance of the pulse transformer. Dynex Application Note AN4840 discusses the use of gate drive load

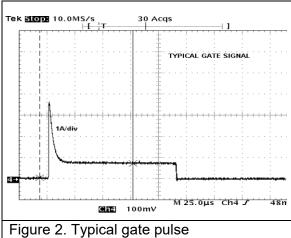lines and the thyristor gate current- gate voltage characteristics.



The duration of the gate pulse has to be long enough for the anode current in the thyristor to reach the Latching Current specified in the datasheet or the thyristor might drop out of conduction when the gate signal is removed. Typically 100µs to 150µs is adequate to allow for delay, turnon and spreading times. However, to reduce the load on the gate driver, the gate current does not need to be maintained at the peak value but can be reduced to a lower level of about 1A known as the back-porch current.

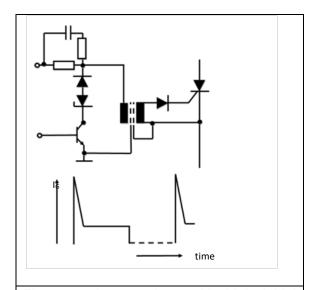


Figure 3. Long pulses with high initial peak

Although with many power circuits a pulse of 100µs to 150µs is sufficient to turn the thyristor on and maintain it in conduction, some circuits require the gate current to continue throughout the conducting period, while in other cases a train of short pulses during the conduction period is sufficient. The voltage may temporarily reverse during the conduction period or there may not be positive volts present at the initial point of firing. In the extreme, in the case of a AC converter with an inductive load for instance, a pulse duration of 180°- □ is required i.e. up to 10ms for 50Hz.The most suitable system depends upon the power circuit being employed. However, the gate should only be made as long as is necessary because the magnitude of the average gate power has to be considered and the longer the gate pulse the higher the average power and hence additional heating and possible destruction of the thyristor.

In practice it is uneconomic to produce gate drives with very long pulses for reasons of power requirements and availability of pulse transformers with suitable inductance. A

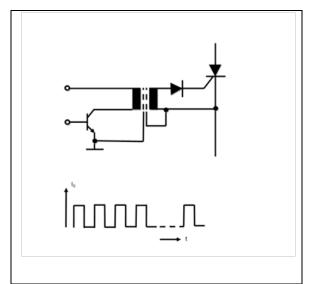


Figure 4. Short pulse picket fence

chain of short pulses with a frequency in the region of 5kHz to 10kHz is often used. This is sometimes called a "picket fence" waveform.

If the gaps between the pulses cause interference, a second time shifted pulse chain can be superimposed to produce a continuous long pulse. The pulse transformer only has to be dimensioned for a single pulse in the chain, say 50µs to 100µs.

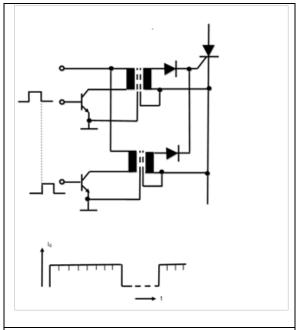


Figure 5. Interleaved pulses

Note that in the above circuits a diode is included between the pulse transformer and the thyristor to eliminate negative gate pulses that are mentioned in the introduction.


Interference

The gate drive is what determines the performance of the equipment. Incorrect firing of the gate drive can lead to disastrous consequences. One of the frequent causes of gate drive mis-firing is interference transmitted into the firing circuit from either the power circuit or from the operation of relays and contactors located in close proximity. It is therefore advisable to incorporate components into the output stage of the gate drive to improve noise immunity. These would include the blocking diodes, capacitors and earth screens on the pulse transformers.

The output circuit of the firing circuit

The typical output circuit would therefore include:

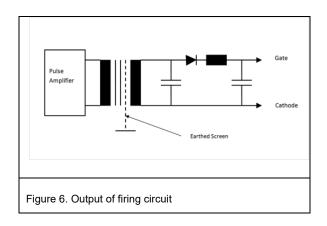- The pulse transformer for circuit isolation
- The resistor to limit the maximum gate current
- The diode, capacitors, and earth screening to prevent spurious triggering.



IMPORTANT INFORMATION:

This publication is provided for information only and not for resale.

The products and information in this publication are intended for use by appropriately trained technical personnel.

Due to the diversity of product applications, the information contained herein is provided as a general guide only and does not constitute any guarantee of suitability for use in a specific application. The user must evaluate the suitability of the product and the completeness of the product data for the application. The user is responsible for product selection and ensuring all safety and any warning requirements are met. Should additional product information be needed please contact Customer Service.

Although we have endeavoured to carefully compile the information in this publication it may contain inaccuracies or typographical errors. The information is provided without any warranty or guarantee of any kind.

This publication is an uncontrolled document and is subject to change without notice. When referring to it please ensure that it is the most up to date version and has not been superseded.

The products are not intended for use in applications where a failure or malfunction may cause loss of life, injury or damage to property. The user must ensure that appropriate safety precautions are taken to prevent or mitigate the consequences of a product failure or malfunction.

The products must not be touched when operating because there is a danger of electrocution or severe burning. Always use protective safety equipment such as appropriate shields for the product and wear safety glasses. Even when disconnected any electric charge remaining in the product must be discharged and allowed to cool before safe handling using protective gloves.

Extended exposure to conditions outside the product ratings may affect reliability leading to premature product failure. Use outside the product ratings is likely to cause permanent damage to the product. In extreme conditions, as with all semiconductors, this may include potentially hazardous rupture, a large current to flow or high voltage arcing, resulting in fire or explosion. Appropriate application design and safety precautions should always be followed to protect persons and property.

Product Status & Product Ordering:

We annotate datasheets in the top right hand corner of the front page, to indicate product status if it is not yet fully approved for production. The annotations are as follows:-

Target Information: This is the most tentative form of information and represents a very preliminary

specification. No actual design work on the product has been started.

Preliminary Information: The product design is complete and final characterisation for volume production is in

progress. The datasheet represents the product as it is now understood but details may

change.

No Annotation: The product has been approved for production and unless otherwise notified by Dynex

any product ordered will be supplied to the current version of the data sheet

prevailing at the time of our order acknowledgement.

All products and materials are sold and services provided subject to Dynex's conditions of sale, which are available on request.

Any brand names and product names used in this publication are trademarks, registered trademarks or trade names of their respective owners.

HEADQUARTERS OPERATIONS

CUSTOMER SERVICE

Phone: +44 (0) 1522 502753 / 502901

e-mail: powersolutions@dynexsemi.com

DYNEX SEMICONDUCTOR LIMITED
Doddington Road, Lincoln, Lincolnshire, LN6 3LF

United Kingdom.

Phone: +44 (0) 1522 500500 Web: http://www.dynexsemi.com

© Dynex Semiconductor Ltd.

Technical Documentation – Not for resale.